The University of Nottingham

UNITED KINGDOM · CHINA · MALAYSIA

Department of Electrical and Electronic Engineering Faculty of Engineering

Practical Engineering Design Solutions and Project Development

(EEEE2046 UNUK) (FYR1 22-23)

# Filter Design Coursework

Author:
George Downing

Student Number:
20273662

October 24, 2022

# Contents

**1 Introduction** **2**
1.1 Background . . . 2
1.2 Butterworth Filter . . . 2
1.3 Chebyshev Filter . . . 2
1.4 Multiple Feedback Filter Topology . . . 2

**2 Results** **2**
2.1 Design requirements and specification . . . 2
2.2 Calculations . . . 2
2.3 Simulation Results . . . 2
2.4 Schematic Design in LTSpice . . . 2

**3 Discussion** **2**
3.1 Calculations for E24 Series Components . . . 2
3.2 Schematic Design for E24 Series Components . . . 2
3.3 Results of Changing to E24 Series Components . . . 2
3.4 Effect of Component Tolerances . . . 2
3.5 Design to Include Additional Amplification . . . 2

**4 Conclusion** **2**

**References** **2**

**Appendices** **2**
A Matlab Code . . . 2
B LTSpice Code . . . 2

# 1 Introduction

## 1.1 Background

## 1.2 Butterworth Filter

## 1.3 Chebyshev Filter

## 1.4 Multiple Feedback Filter Topology

# 2 Results

## 2.1 Design requirements and specification

## 2.2 Calculations

## 2.3 Simulation Results

## 2.4 Schematic Design in LTSpice

# 3 Discussion

## 3.1 Calculations for E24 Series Components

## 3.2 Schematic Design for E24 Series Components

## 3.3 Results of Changing to E24 Series Components

## 3.4 Effect of Component Tolerances

## 3.5 Design to Include Additional Amplification

# 4 Conclusion

# References

# Appendices

## A Matlab Code

## B LTSpice Code